

Total number of printed pages-4

44 (2) BCA-HG-2016

2024

## BASIC ELECTRONICS

Paper : BCA-HG-2016

Full Marks : 80

Time : Three hours

***The figures in the margin indicate full marks for the questions.***

1. Fill in the blanks : 1×8=8

(a) The binary number 10101 is equivalent to decimal number \_\_\_\_.

(b) The unit of resistances is \_\_\_\_.

(c) The knee voltage for silicon *p-n* junction is \_\_\_\_ volt.

(d) Diode is used as a \_\_\_\_.

(e) The octal number system has a base of \_\_\_\_.

Contd.

- (f) Oscillator employs \_\_\_\_\_ feedback.
- (g) The main function of a capacitor is \_\_\_\_\_.
- (h) A transistor has \_\_\_\_\_ terminals.

2. Answer the following questions in short :  
2×6=12

- (a) Write *two* properties of semiconductor materials.
- (b) What do you mean by forward and reverse biasing of a *p-n* junction diode ?
- (c) Draw the symbol of NPN transistor and specify the terminals.
- (d) Write *two* applications of flip-flop.
- (e) Write the truth table of an exclusive OR (XOR) gate.
- (f) How will you obtain NOT gate from NAND gate ?

3. Answer **any four** questions from the following :  
5×4=20

- (a) Draw and explain the V-I characteristic of a *p-n* junction diode.

(b) Explain the basic laws of Boolean algebra.

(c) What do you mean by minterm and maxterm? Draw the logic diagram of the following :

$$Y = (A + BC)(B + \bar{C}A)$$

(d) Design a S-R flip-flop using NAND gates. Write its truth table.

(e) Mention some advantages of negative feedback.

(f) Describe briefly different types of filters.

(g) Explain briefly the working of a NPN transistor.

(h) Simplify the Boolean function :

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$$

4. Answer **any three** of the following questions : 10×3=30

(a) What are different transistor configuration? Explain CE configuration with neat diagram.



(b) What is a flip-flop ? What are different types of flip-flops ? Design a 3-bit counter using flip-flops.

(c) Explain with a neat diagram, the working of a bridge rectifier.

(d) What is shift register ? What are the applications of shift register ? Design a shift register using flip-flops.

5. Write short notes on **any two** of the following :  
 $5 \times 2 = 10$

(a) Universal logic gates

(b) Capacitors

(c) Multiplexer

(d) Oscillators

---