

Total number of printed pages-4

44 (2) BCA-2·3

2023

DIGITAL LOGIC FUNDAMENTALS

Paper : BCA-2·3

Full Marks : 80

Time : Three hours

The figures in the margin indicate full marks for the questions.

1. Fill in the blanks with appropriate words :
1×5=5

(i) For a 2 input logic gate the output will be 1 when both the inputs are 1 is _____ gate.

(ii) Flip-flop is a _____ circuit.

(iii) The _____ gate is known as a universal logic gate.

(iv) $x \cdot x =$ _____ .

Contd.

(v) The POS in Boolean logic stands for _____ .

2. Answer **any five** questions from the following : 2×5=10

(a) Draw the symbol and give the truth table of NOR gate.

(b) Explain De Morgan's theorem.

(c) Explain state table.

(d) Mention *two* examples of combinational circuit.

(e) What are the main *two* types of sequential circuit? Define.

(f) What is ADDER? Define its types.

(g) What do you mean by shift register?

3. Answer **any four** questions from the following : 5×4=20

(a) What are the different types of shift registers used in digital system design? Explain briefly.

- (b) Show that $x + x = x$.
- (c) Write a short note on the different postulates and basic theorems of Boolean algebra.
- (d) What is Demultiplexer? Draw the logic diagram.
- (e) Explain the working of Encoder.
- (f) Simplify the Boolean function
 $F(w, x, y, z) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
4. (a) What is a counter? Design a 3-bit binary counter and give logic diagram.
2+8=10

Or

What is JK flip-flop? Write the truth table of a JK flip-flop and discuss its operation.

- (b) What do you mean by parallel load? Explain the working and design of a registers with parallel load. 2+8=10

Or

Explain the working of Magnitude comparator.

5. (a) What is excitation tables? Give excitation table for RS flip-flop.

2+3=5

(b) Using De Morgan's theorem show that $A + A'B + A'B' = 1$.

5

Or

Given the Boolean function

$$F = xy'z + x'y'z + xyz$$

Draw the logic diagram using the original Boolean expression.

6. Write short notes on : **(any three)**

5×3=15

(a) Multiplexer

(b) State reduction and Assignment

(c) D flip-flop

(d) Binary ripple counter

(e) State diagram and state equation